

# Contents

*Preface* v

*Acknowledgments* vi

*A Note to the Student* ix

## PART I | DC CIRCUITS |

<b>Chapter 1</b>	<b>Basic Concepts</b>	<b>3</b>
1.1	Introduction	4
1.2	Systems of Units	4
1.3	Charge and Current	6
1.4	Voltage	9
1.5	Power and Energy	10
1.6	Circuit Elements	13
†1.7	Applications	15
1.7.1	TV Picture Tube	
1.7.2	Electricity Bills	
†1.8	Problem Solving	18
1.9	Summary	21
Review Questions	22	
Problems	23	
Comprehensive Problems	25	
<b>Chapter 2</b>	<b>Basic Laws</b>	<b>27</b>
2.1	Introduction	28
2.2	Ohm's Laws	28
†2.3	Nodes, Branches, and Loops	33
2.4	Kirchhoff's Laws	35
2.5	Series Resistors and Voltage Division	41
2.6	Parallel Resistors and Current Division	42
†2.7	Wye-Delta Transformations	50
†2.8	Applications	54
2.8.1	Lighting Systems	
2.8.2	Design of DC Meters	
2.9	Summary	60
Review Questions	61	
Problems	63	
Comprehensive Problems	72	
<b>Chapter 3</b>	<b>Methods of Analysis</b>	<b>75</b>
3.1	Introduction	76
3.2	Nodal Analysis	76
3.3	Nodal Analysis with Voltage Sources	82
3.4	Mesh Analysis	87
3.5	Mesh Analysis with Current Sources	92
†3.6	Nodal and Mesh Analyses by Inspection	95

3.7	Nodal Versus Mesh Analysis	99
3.8	Circuit Analysis with <i>PSpice</i>	100
†3.9	Applications: DC Transistor Circuits	102
3.10	Summary	107

Review Questions	107
Problems	109
Comprehensive Problems	117

<b>Chapter 4</b>	<b>Circuit Theorems</b>	<b>119</b>
4.1	Introduction	120
4.2	Linearity Property	120
4.3	Superposition	122
4.4	Source Transformation	127
4.5	Thevenin's Theorem	131
4.6	Norton's Theorem	137
†4.7	Derivations of Thevenin's and Norton's Theorems	140
4.8	Maximum Power Transfer	142
4.9	Verifying Circuit Theorems with <i>PSpice</i>	144
†4.10	Applications	147
4.10.1	Source Modeling	
4.10.2	Resistance Measurement	
4.11	Summary	153
Review Questions	153	
Problems	154	
Comprehensive Problems	162	

<b>Chapter 5</b>	<b>Operational Amplifiers</b>	<b>165</b>
5.1	Introduction	166
5.2	Operational Amplifiers	166
5.3	Ideal Op Amp	170
5.4	Inverting Amplifier	171
5.5	Noninverting Amplifier	174
5.6	Summing Amplifier	176
5.7	Difference Amplifier	177
5.8	Cascaded Op Amp Circuits	181
5.9	Op Amp Circuit Analysis with <i>PSpice</i>	183
†5.10	Applications	185
5.10.1	Digital-to-Analog Converter	
5.10.2	Instrumentation Amplifiers	
5.11	Summary	188
Review Questions	190	
Problems	191	
Comprehensive Problems	200	

<b>Chapter 6</b>	<b>Capacitors and Inductors</b>	<b>201</b>
6.1	Introduction	202
6.2	Capacitors	202
6.3	Series and Parallel Capacitors	208
6.4	Inductors	211
6.5	Series and Parallel Inductors	216
†6.6	Applications	219
6.6.1	Integrator	
6.6.2	Differentiator	
6.6.3	Analog Computer	
6.7	Summary	225
	Review Questions	226
	Problems	227
	Comprehensive Problems	235
<b>Chapter 7</b>	<b>First-Order Circuits</b>	<b>237</b>
7.1	Introduction	238
7.2	The Source-free $RC$ Circuit	238
7.3	The Source-free $RL$ Circuit	243
7.4	Singularity Functions	249
7.5	Step Response of an $RC$ Circuit	257
7.6	Step Response of an $RL$ Circuit	263
†7.7	First-order Op Amp Circuits	268
7.8	Transient Analysis with $PSpice$	273
†7.9	Applications	276
7.9.1	Delay Circuits	
7.9.2	Photoflash Unit	
7.9.3	Relay Circuits	
7.9.4	Automobile Ignition Circuit	
7.10	Summary	282
	Review Questions	283
	Problems	284
	Comprehensive Problems	293
<b>Chapter 8</b>	<b>Second-Order Circuits</b>	<b>295</b>
8.1	Introduction	296
8.2	Finding Initial and Final Values	296
8.3	The Source-Free Series $RLC$ Circuit	301
8.4	The Source-Free Parallel $RLC$ Circuit	308
8.5	Step Response of a Series $RLC$ Circuit	314
8.6	Step Response of a Parallel $RLC$ Circuit	319
8.7	General Second-Order Circuits	322
8.8	Second-Order Op Amp Circuits	327
8.9	$PSpice$ Analysis of $RLC$ Circuits	330
†8.10	Duality	332
†8.11	Applications	336
8.11.1	Automobile Ignition System	
8.11.2	Smoothing Circuits	

8.12	Summary	340
	Review Questions	340
	Problems	341
	Comprehensive Problems	350

<b>PART 2</b>	<b>AC CIRCUITS</b>	<b>351</b>
<b>Chapter 9</b>	<b>Sinusoids and Phasors</b>	<b>353</b>
9.1	Introduction	354
9.2	Sinusoids	355
9.3	Phasors	359
9.4	Phasor Relationships for Circuit Elements	367
9.5	Impedance and Admittance	369
9.6	Kirchhoff's Laws in the Frequency Domain	372
9.7	Impedance Combinations	373
†9.8	Applications	379
9.8.1	Phase-Shifters	
9.8.2	AC Bridges	
9.9	Summary	384
	Review Questions	385
	Problems	385
	Comprehensive Problems	392
<b>Chapter 10</b>	<b>Sinusoidal Steady-State Analysis</b>	<b>393</b>
10.1	Introduction	394
10.2	Nodal Analysis	394
10.3	Mesh Analysis	397
10.4	Superposition Theorem	400
10.5	Source Transformation	404
10.6	Thevenin and Norton Equivalent Circuits	406
10.7	Op Amp AC Circuits	411
10.8	AC Analysis Using $PSpice$	413
†10.9	Applications	416
10.9.1	Capacitance Multiplier	
10.9.2	Oscillators	
10.10	Summary	420
	Review Questions	421
	Problems	422
<b>Chapter 11</b>	<b>AC Power Analysis</b>	<b>433</b>
11.1	Introduction	434
11.2	Instantaneous and Average Power	434
11.3	Maximum Average Power Transfer	440
11.4	Effective or RMS Value	443
11.5	Apparent Power and Power Factor	447
11.6	Complex Power	449
†11.7	Conservation of AC Power	453

11.8	Power Factor Correction	457
†11.9	Applications	459
11.9.1	Power Measurement	
11.9.2	Electricity Consumption Cost	
11.10	Summary	464
	Review Questions	465
	Problems	466
	Comprehensive Problems	474

## Chapter 12 Three-Phase Circuits 477

12.1	Introduction	478
12.2	Balanced Three-Phase Voltages	479
12.3	Balanced Wye-Wye Connection	482
12.4	Balanced Wye-Delta Connection	486
12.5	Balanced Delta-Delta Connection	488
12.6	Balanced Delta-Wye Connection	490
12.7	Power in a Balanced System	494
†12.8	Unbalanced Three-Phase Systems	500
12.9	<i>PSpice</i> for Three-Phase Circuits	504
†12.10	Applications	508
12.10.1	Three-Phase Power Measurement	
12.10.2	Residential Wiring	
12.11	Summary	516
	Review Questions	517
	Problems	518
	Comprehensive Problems	525

## Chapter 13 Magnetically Coupled Circuits 527

13.1	Introduction	528
13.2	Mutual Inductance	528
13.3	Energy in a Coupled Circuit	535
13.4	Linear Transformers	539
13.5	Ideal Transformers	545
13.6	Ideal Autotransformers	552
†13.7	Three-Phase Transformers	556
13.8	<i>PSpice</i> Analysis of Magnetically Coupled Circuits	559
†13.9	Applications	563
13.9.1	Transformer as an Isolation Device	
13.9.2	Transformer as a Matching Device	
13.9.3	Power Distribution	
13.10	Summary	569
	Review Questions	570
	Problems	571
	Comprehensive Problems	582

## Chapter 14 Frequency Response 583

14.1	Introduction	584
14.2	Transfer Function	584
†14.3	The Decibel Scale	588

14.4	Bode Plots	589
14.5	Series Resonance	600
14.6	Parallel Resonance	605
14.7	Passive Filters	608
14.7.1	Lowpass Filter	
14.7.2	Highpass Filter	
14.7.3	Bandpass Filter	
14.7.4	Bandstop Filter	
14.8	Active Filters	613
14.8.1	First-Order Lowpass Filter	
14.8.2	First-Order Highpass Filter	
14.8.3	Bandpass Filter	
14.8.4	Bandreject (or Notch) Filter	
†14.9	Scaling	619
14.9.1	Magnitude Scaling	
14.9.2	Frequency Scaling	
14.9.3	Magnitude and Frequency Scaling	
14.10	Frequency Response Using <i>PSpice</i>	622
†14.11	Applications	626
14.11.1	Radio Receiver	
14.11.2	Touch-Tone Telephone	
14.11.3	Crossover Network	
14.12	Summary	631
	Review Questions	633
	Problems	633
	Comprehensive Problems	640

## PART 3 ADVANCED CIRCUIT ANALYSIS 643

### Chapter 15 The Laplace Transform 645

15.1	Introduction	646
15.2	Definition of the Laplace Transform	646
15.3	Properties of the Laplace Transform	649
15.4	The Inverse Laplace Transform	659
15.4.1	Simple Poles	
15.4.2	Repeated Poles	
15.4.3	Complex Poles	
15.5	Application to Circuits	666
15.6	Transfer Functions	672
15.7	The Convolution Integral	677
†15.8	Application to Integrodifferential Equations	685
†15.9	Applications	687
15.9.1	Network Stability	
15.9.2	Network Synthesis	
15.10	Summary	694

Review Questions	696
Problems	696
Comprehensive Problems	705

## Chapter 16 The Fourier Series 707

16.1	Introduction	708
16.2	Trigonometric Fourier Series	708
16.3	Symmetry Considerations	717
16.3.1	Even Symmetry	
16.3.2	Odd Symmetry	
16.3.3	Half-Wave Symmetry	
16.4	Circuit Applications	727
16.5	Average Power and RMS Values	730
16.6	Exponential Fourier Series	734
16.7	Fourier Analysis with <i>PSpice</i>	740
16.7.1	Discrete Fourier Transform	
16.7.2	Fast Fourier Transform	
†16.8	Applications	746
16.8.1	Spectrum Analyzers	
16.8.2	Filters	
16.9	Summary	749

Review Questions	751
Problems	751
Comprehensive Problems	758

## Chapter 17 Fourier Transform 759

17.1	Introduction	760
17.2	Definition of the Fourier Transform	760
17.3	Properties of the Fourier Transform	766
17.4	Circuit Applications	779
17.5	Parseval's Theorem	782
17.6	Comparing the Fourier and Laplace Transforms	784
†17.7	Applications	785
17.7.1	Amplitude Modulation	
17.7.2	Sampling	

## 17.8 Summary 789

Review Questions	790
Problems	790
Comprehensive Problems	794

## Chapter 18 Two-Port Networks 795

18.1	Introduction	796
18.2	Impedance Parameters	796
18.3	Admittance Parameters	801
18.4	Hybrid Parameters	804
18.5	Transmission Parameters	809
†18.6	Relationships between Parameters	814
18.7	Interconnection of Networks	817
18.8	Computing Two-Port Parameters Using <i>PSpice</i>	823
†18.9	Applications	826
18.9.1	Transistor Circuits	
18.9.2	Ladder Network Synthesis	

## 18.10 Summary 833

Review Questions	834
Problems	835
Comprehensive Problems	844

## Appendix A Solution of Simultaneous Equations Using Cramer's Rule 845

## Appendix B Complex Numbers 851

## Appendix C Mathematical Formulas 859

## Appendix D *PSpice* for Windows 865

## Appendix E Answers to Odd-Numbered Problems 893

## Selected Bibliography 929

## Index 933